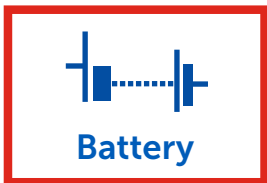



Circuits

There is so much to learn about electricity.


Label the circuit below.




Battery

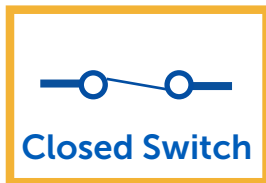


Closed Switch

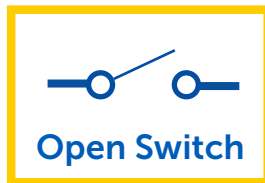

Open Switch

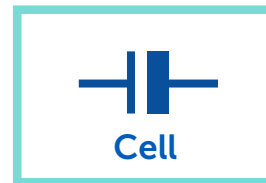


Cell

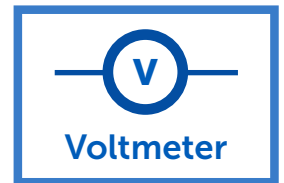


Voltmeter




Buzzer

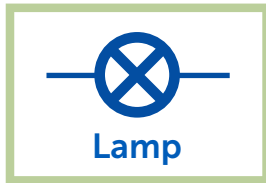


Lamp

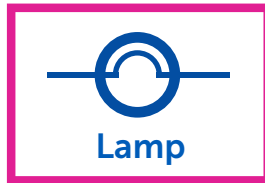


Lamp

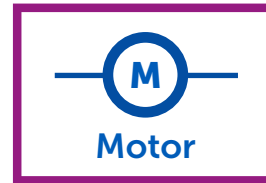

Motor

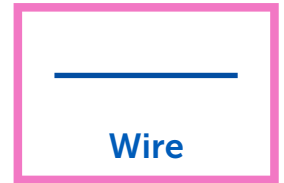


Wire

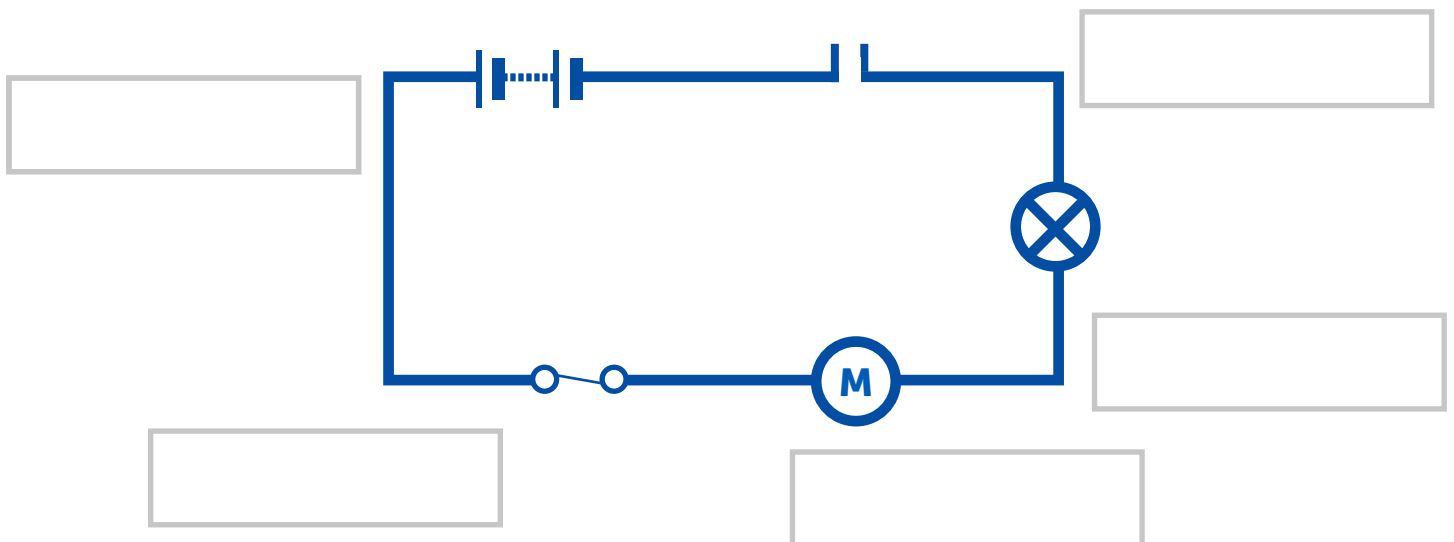



Circuits

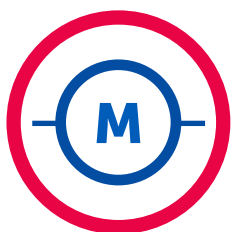

In a circuit, what does this symbol represent?




A motor



A buzzer



A doorbell

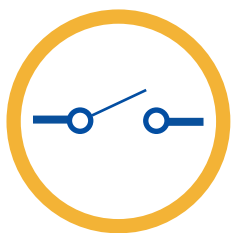

In a circuit, what does this symbol represent?



Open
switch



Broken
switch



Closed
switch




Does this symbol represent a lightbulb?



Yes



No

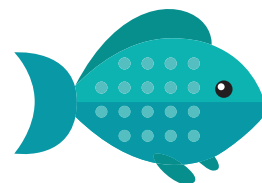



Energy Education Centre

Worksheet

Circuits

Draw a circuit showing a battery powered lightbulb that is currently switched off.

